

Note : Question number 1 is compulsory. Answer any Four questions from the rest. Assume suitable missing data, if any. All abbreviations have their usual meaning.

- Q1. (a) If the emitter current of a transistor is 10 mA and the base current is 1/100 of collector current, determine the values of small-signal model parameters g_m and r_{π} of the transistor. 2
- (b) Find the drain voltage for a fixed bias JFET circuit having $V_{GS} = -3V$, assuming $I_{DSS} = 10mA$, $V_P = -5V$, $V_{DD} = 15V$ and $R_D = 5K\Omega$? 2
- (c) Explain the Barkhausen criterion of sustained oscillation. 2
- (d) Determine the gain desensitivity factor for a feedback amplifier having open loop gain $A = 10^4$ and closed loop gain $A_f = 10^3$. 2

- Q2. (a) For the circuit shown in Fig. 1 determine the value of V_C and I_E if $\beta_F = 100$. 4

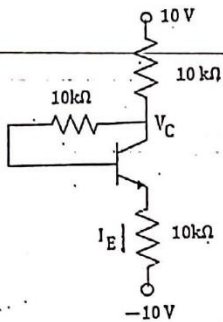


Fig. 1

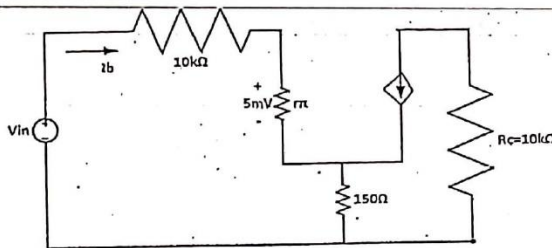


Fig. 2

- (b) Analyze the circuit shown in Fig 2 and determine the input voltage (V_{in}) if the bias current $I_{CQ} = 0.5$ mA and $\beta_F = \beta_0 = 100$. 4

- Q3. (a) An enhancement type NMOSFET with $V_t = 2V$, has its source terminal grounded and a 3V DC source connected to gate. Determine the region of operation of the device for $V_D = 1V$ and the value of drain current if $\mu_n C_{ox} = 20 \mu A/V^2$ and $W/L = 100\mu m/10 \mu m$. 3

Confid - 2

(b) Drawing the small signal circuit of CG amplifier determine the voltage gain, and input resistance of the amplifier 5

Q4. (a) Deduce the expression for input resistance for a shunt-shunt feedback amplifier. 3

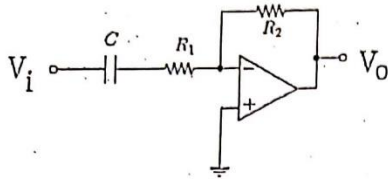


Fig. 3

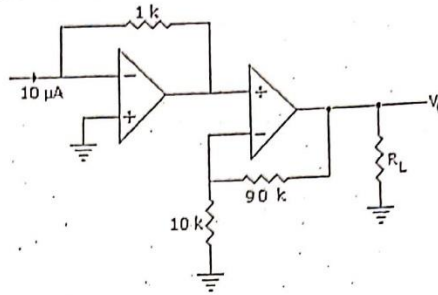


Fig. 4

(b) Derive the transfer function (V_o/V_i) for the circuit shown in Fig. 3. 3

(c) For the circuit shown in Fig. 4 determine the value of output voltage V_o . 2

Q5. (a) An enhancement type NMOSFET with $V_t=2V$, has its source terminal grounded and a 3V DC source connected to gate. Determine the region of operation of the device for $V_D=1V$ and the value of drain current if $\mu_n C_{ox}=20 \mu A/V^2$ and $W/L=100\mu m/10 \mu m$. 3

(b) Drawing the small signal circuit of CG amplifier determine the voltage gain, and input resistance of the amplifier 5

Q6. For the transistor amplifier shown in Fig. 5 assume $R_1 = 16 k\Omega$, $R_2 = 9 k\Omega$, $R_C = 1k\Omega$, and $R_E = 100 \Omega$, $V_{CC} = 2.5V$ and $\beta_F = \beta_0 = 100$.

(a) Determine the Q point and identify the region-of-operation of transistor. 4

(b) Determine voltage gain (V_o/V_s) and input resistance (R_i) for the amplifier. 4

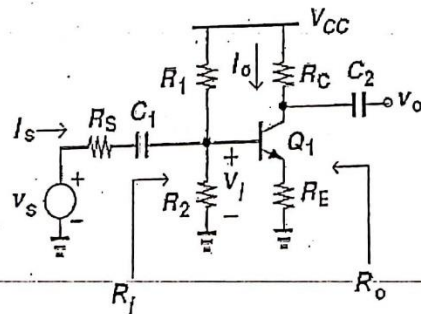


Fig.5

(a)

-84-

or an NMOSFET with $L = 0.18 \mu\text{m}$, $W = 2 \mu\text{m}$, $C_{ox} = 0.2$

$$C_{ox} = 8.6 \text{ fF}/\mu\text{m}^2, \mu_n = 450 \text{ cm}^2/\text{V}\cdot\text{s}, V_T = 0.5 \text{ V},$$

Find V_{GS} & V_{DS} that results in NMOSFET operating at the edge of saturation with $I_D = 100 \mu\text{A}$.

(b) Common drain

Draw the small signal circuit of CD amplifier determine the voltage gain and input resistance of the amplifier.

(c) (a)

For an NMOSFET with $L = 0.18 \mu\text{m}$, $W = 2 \mu\text{m}$, $C_{ox} = 0.2$

$$C_{ox} = 8.6 \text{ fF}/\mu\text{m}^2, \mu_n = 450 \text{ cm}^2/\text{V}\cdot\text{s}, V_T = 0.5 \text{ V},$$

Find V_{GS} & V_{DS} that results in NMOSFET operating at the edge of saturation with $I_D = 100 \mu\text{A}$.

(b) Common drain

Draw the small signal circuit of CD amplifier determine the voltage gain and input resistance of the amplifier.