

Note : Attempt any FIVE questions in All. All questions carry equal marks.

- Q.1(a) Explain the characteristics of
 (i) Ideal and Practical voltage source (4)
 (ii) Ideal and Practical current source (4)
- (b) Reduce the following network shown in Fig.1 to the simplest form which consists of only single voltage source using source transformation technique. (4)

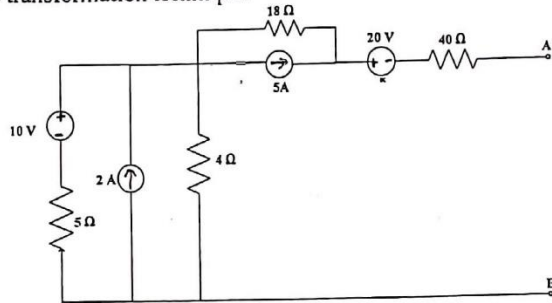


Fig. 1

- Q.2 (a) Obtain the expression of equivalent resistances in delta(Δ) of a given star (Y) connected resistances. (4)
 (b) State Maximum Power Transfer theorem and illustrate with the help of an example. (4)
- Q.3 (a) State Superposition theorem. Explain its advantages and limitations. (4)
 (b) Determine the Thevenin equivalent circuit as seen from terminals cd for the circuit shown in Fig. 2. (4)

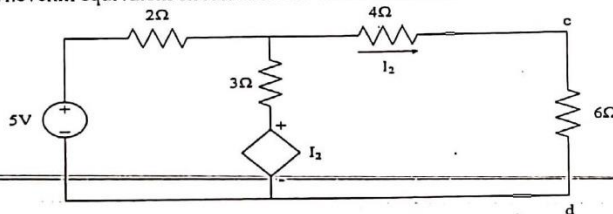


Fig. 2

- Q.4(a) How is the effective value determined for nonsinusoidal waveform? Determine the rms value of a resultant current in a wire carrying simultaneously a direct current of 10A and a sinusoidal current of peak value of 10 A. (4)
 (b) A series circuit consists of 1200 Ω resistor, a 1.0 H coil, and a capacitor C. Determine the value of C and the bandwidth of the circuit if the resonant frequency is 4 kHz. (4)
- Q.5 (a) Explain with phasor diagram the measurement of the power and pf of a balanced three phase load with the help of two wattmeter method. (4)
 (b) A 400 V, 3 phase supply is connected across a balanced network of three impedances each consisting of a 32 Ω resistance and 24 Ω inductive reactance. Determine the line current and power factor when the impedances are connected in delta. Draw the phasor diagram showing phase voltages, line voltages and currents. (4)
- Q.6 (a) Draw the analogy between electric and magnetic circuits. State and explain Kirchhoff's laws for magnetic circuits. (4)
 (b) What are the various losses in a transformer? Explain with the help of circuit diagram the tests needed to determine these losses. (4)
- Q. 7 Write short notes on any two of the following: (4x2)
 (i) Shunt and multipliers for instruments (ii) Autotransformer
 (iii) PMMC instruments (iv) Digital Voltmeter