

Total No. of Page – 02

-113-

Roll No.

V Semester EE/EL

B.Tech

Supplementary Examination

February – 2019

EL/EE-301 Power Electronics

Time: 3:00 Hours

Max. Marks: 40

Note: Question No. 1 is compulsory. Attempt any four from the remaining questions.
Assume suitable missing data, if any.

Q.1 Answer in brief: -

(a) Draw the symbol and VI characteristics of the GTO. [1]

(b) Why doesn't IGBT exhibit secondary break-down phenomenon? [1]

(c) Why is high interdigitation of the gate design preferred in GTO? [1]

(d) Draw the thermal equivalent circuit of SCR and list the various parameters involved in it. [1]

(e) A single phase voltage controller is connected to a load of resistance 10Ω and a supply of $200 \sin 314t$ volts. Find the average thyristor current for a firing angle of $\frac{\pi}{2}$ [1]

(f) Why is the switching frequency of MOSFET higher than that of other semiconductor devices? [1]

(g) A single phase full wave mid-point thyristor converter uses a 230/200 V transformer with centre tap on the secondary side. Find the peak inverse voltage of the thyristor. [1]

(h) What are the effects of high $\frac{dv}{dt}$ and high $\frac{di}{dt}$ on an SCR? [1]

Q.2 (a) Describe various types of power diodes indicating clearly the differences amongst them. [4]

(b) Draw the switching characteristics of a thyristor during its' turn-on and turn-off processes. Show the variation of voltage across the thyristor and the current through it during switching and also indicate the various time intervals of turn-on and turn-off times. [4]

Q.3 (a) A single phase full converter is supplied from a 230V, 50Hz source. The load consists of $R=10\Omega$ and a large inductance so as to render the load current constant. For a firing angle of 30° , determine: [4]

(i) average output voltage and average output current.

(ii) average thyristor current and rms thyristor current.

P. T. O

- (b) Describe the operating principle of a single phase to single phase step up cyclo-converter with the help of a bridge configuration. Also draw the appropriate circuit and wave forms. [4]
- Q.4 (a) A single phase semi-converter feeds power to RLE load. Draw the source voltage, output voltage, load current, source current and free-wheeling diode current waveforms as a function of time when the extinction angle $\beta > \pi$. [4]
- (b) Explain how the step up chopper can be used for regenerative braking of motors with suitable circuit diagram and waveforms. [4]
- Q.5 (a) A three - phase full converter is operated from a three - phase star connected 208V, 60Hz supply and the load resistance is $R=10\Omega$. If it is required to obtain an average output voltage of 50% of the maximum possible output voltage, calculate: - [4]
- (i) The firing delay angle α .
 - (ii) The rms and average output currents.
 - (iii) The rms and average thyristor currents.
 - (iv) The rectification efficiency.
- (b) A Type A chopper feeds power to an RLE load with $R=2\Omega$, $L=10\text{mH}$ and $E=6\text{V}$. [4]
If this chopper is operating at a chopping frequency of 1kHz and duty cycle of 10% from a 220V DC source, compute the maximum and minimum currents drawn by the load.
- Q.6 (a) Determine the Fourier Series expression for the output voltage and current [4]
obtained from a single phase half bridge inverter.
- (b) A single phase voltage controller feeds power to a resistive load of 3Ω from a [4]
230V, 50Hz source. Calculate: -
- (i) The maximum values of average and rms thyristor current for any firing angle α .
 - (ii) The minimum circuit turn off time for any firing angle α .
 - (iii) The ratio of third harmonic voltage to fundamental voltage for $\alpha = \frac{\pi}{3}$
- Q.7 (a) Discuss the principle of working of a three-phase bridge inverter using an [4]
appropriate circuit diagram. Draw the phase and line voltage wave forms on the assumption that each thyristor conducts for 180° and the resistive load is star-connected.
- (b) For a single pulse modulation used in inverters with pulse width = $2d$, show [4]
that the output voltage can be expressed as

$$v_0 = \sum_{\alpha=1,3,5}^{\infty} \frac{4V_s}{n\pi} \cdot \sin \frac{n\pi}{2} \cdot \sin nd \cdot \sin n\omega t$$