

Note: Question number 1 is compulsory. Answer any four questions from the rest. Any required data not explicitly given, may be suitably assumed. Use the answer sheet judiciously. Symbols have their usual meanings.

Q6. (a) Determine the $i(t)$ and $v_L(t)$ valid for $t > 0$ in the circuit of Fig. 6(a)

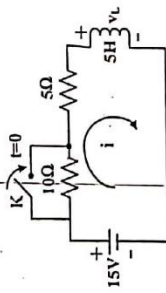


Fig. 6(a)

(b) The complete incidence matrix of a planar graph is given below:

Branches →	1	2	3	4	5	6
Nodes ↓	0	1	0	-1	-1	1
	0	-1	1	0	1	0
	-1	0	0	1	0	-1
	1	0	-1	0	0	0

Draw the oriented graph. Define branch, node, tree, co-tree, twig and link with examples.

-END-

Q1. Choose the correct or best alternative in the following: 10

(i) In order that $f(t)$ be Laplace transformable, it is sufficient that:

(a) $\int_0^{\infty} |f(t)| e^{-\sigma t} dt > \infty$ (b) $\int_0^{\infty} |f(t)| e^{\sigma t} dt < \infty$ (c) $\int_0^{\infty} |f(t)| e^{-\sigma t} dt < \infty$

(d) some other answer

(ii) The derivative of the unit ramp function is the:

(a) unit step (b) unit impulse (c) doublet (d) some other answer

(iii) Which of the circuits shown in Fig. 1(iii) are characterized by the equation $v(t) = Ri(t)$:

(a) circuit 1 (b) circuit 2 (c) circuit 3 (d) some other answer

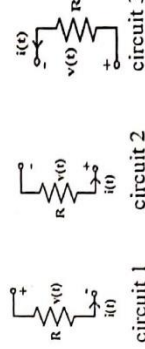


Fig.1(iii)

(iv) The poles and zeros of a positive real function :

(a) Must be in right half of the s plane

(b) Must be in left half of the s plane

(c) Can be anywhere in the s plane

(d) None of the above

(v) The number of twigs, in any selected tree of a graph with 'b' branches and 'n' nodes is:

(a) (n-1) (b) (b-n+1) (c) n (d) (b-n)

(vi) A two-port network is symmetrical if:

(a) $Z_{11}Z_{22} - Z_{12}Z_{21} = 1$ (b) $h_{11}h_{22} - h_{12}h_{21} = 1$ (c) $g_{11}g_{22} - g_{12}g_{21} = 1$

P.T.O

(d) $AD - BC = 1$

(vii) The input impedance of an LC network must have:

- (a) a zero at infinity (b) a pole at infinity (c) either a pole or a zero at infinity (d) neither a pole nor a zero at infinity

(viii) $\text{Re}[Z_{in}(j\omega)]$ is a:

- (a) monotonically increasing function of ω (b) monotonically decreasing function of ω (c) positive real constant (d) maximum at a non-zero finite frequency

(ix) The value of current i in the circuit of Fig.1(ix):

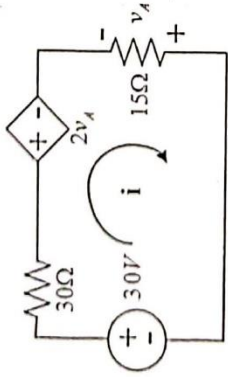


Fig.1(ix)

- (a) 1A (b) 3A (c) 2A (d) 0.5A

(x) Suppose $V_c(t) = \sin(40t + \frac{\pi}{6})V$. The value of $i_c(t)$ in Fig. 1(x) is:

- (a) $10\cos(40t + \frac{\pi}{6})A$ (b) $40\cos(20t + \frac{\pi}{6})A$ (c) $10\sin(20t + \frac{\pi}{6})A$ (d) $20\sin(40t + \frac{\pi}{6})A$



Fig.1(x)

Q2. (a) Derive the inter-relationship between z parameters and h parameters. 5

(b) Calculate the maximum power that can be delivered to the Load (R_L) for the circuit given in Fig.2(b). 5

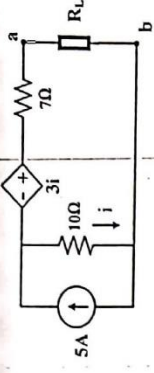


Fig.2(b)

Q3. Find the expression for $v_c(t)$ and $v_L(t)$ in the circuit of Fig.3, valid for all time t . 10

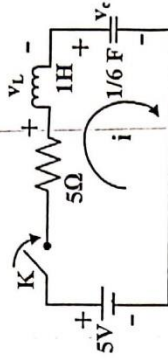


Fig.3

Q4. Which of the following functions is LC driving point impedance? 10

$$Z_1(s) = \frac{s(s^2+4)(s^2+16)}{(s^2+9)(s^2+25)}$$

$$Z_2(s) = \frac{(s^2+1)(s^2+3)}{s(s^2+2)}$$

$$Z_3(s) = \frac{s(s+3)}{(s+1)(s+5)}$$

Give justification and synthesize the realizable impedance in second Foster form (parallel) and first Cauer form.

Q5. Which of the following functions is RC driving point impedance? 10

$$Z_1(s) = \frac{(s+1)(s+3)}{s(s+2)}$$

$$Z_2(s) = \frac{2(s+1)(s+6)}{(s+2)(s+3)}$$

$$Z_3(s) = \frac{(s^2+1)(s^2+16)}{s(s^2+9)}$$

Give justification and synthesize the realizable impedance in one of the Foster form and one of the Cauer form