

Total No. of Pages: 03

Roll No. ....

B. Tech. (ME) Evening

FIRST SEMESTER

SUPPLEMENTARY EXAMINATION

(FEB-2019)

CEE 105 ELECTRICAL TECHNOLOGY

Time: 3 Hours

Max. Marks: 40

Note: Answer five questions. Question No. 1 is compulsory. Each question carry equal marks. Assume the missing data suitably (if any).

1. State true and false. Also, justify your answer with the help of suitable example/diagram (if any). [8x1=8]
- (a) The superposition theorem is applicable for linear and non-linear circuits.
- (b) The value peak factor can be determined with the help of peak value and average value of an alternating quantity.
- (c) In series resonance, the frequency corresponding to maximum value of current is known as resonant frequency.
- (d) If the copper and core losses in a transformer at half load is 50 W and 30 W respectively, then the copper loss and core loss at full load would be 100 W and 30 W respectively.
- (e) The distribution transformers are designed for approximately 100% efficiency.
- (f) An incandescent lamp of 100 W is operated for 10 hours/day. The energy consumed in 1 month will be 3 kWh.
- (g) In three phase star connected system, the reactive power can be calculated using  $3V_p I_p \cos \theta$
- (h) The slip of three phase induction motor is determined using the relation  $(N_s - N_r)/N_s$ .

1-232-

P.T.O

2 (a) State and explain maximum power transfer theorem. Derive the condition of maximum power transfer. Also write down the applications of maximum power transfer theorem. [4]

(b) State and explain Thevenin's theorem. Determine the current in  $25\ \Omega$  resistance of the network shown in Fig. 1. using Thevenin's theorem. [4]

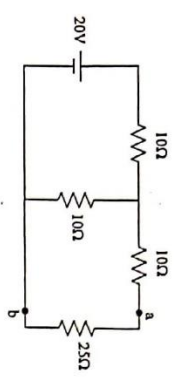


Fig. 1.

3 (a) Find the impedance, power factor and current in each branch of the network shown in Fig. 2. [4]

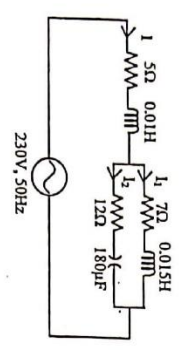


Fig. 2.

(b) A coil having a resistance of  $8\ \Omega$  and an inductance of  $0.05\ \text{H}$  is connected across a  $230\ \text{V}$ ,  $50\ \text{Hz}$  supply. Calculate the current, phase angle, apparent power, active and reactive power. [4]

4 (a) In a three phase, 4 wire system as shown in Fig. 3, the line voltage is  $415\ \text{V}$  and non-inductive load of  $10\ \text{kW}$ ,  $8\ \text{kW}$  and  $5\ \text{kW}$  are connected between the three-line conductors and neutral. Calculate (i) the current in each line (ii) the current in the neutral conductor [4]

P.T.O

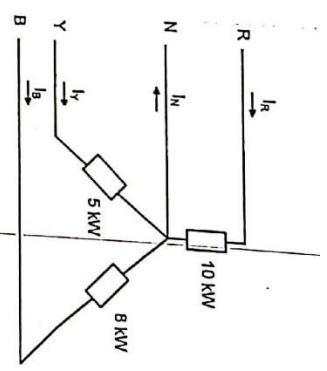


Fig. 3.

(b) Derive the relation between phase and line voltages, and phase and line currents for balanced three phase load when (i) star connected (ii) delta connected. [4]

5 (a) The primary and secondary windings of a  $500\text{-kVA}$  transformer have a resistance of  $0.42\ \Omega$  and  $0.0019\ \Omega$  respectively. The primary and secondary voltages are  $11000\ \text{V}$  and  $400\ \text{V}$  respectively and the core loss is  $2.9\ \text{kW}$ , assuming the power factor of the load to be  $0.8$ . Calculate the efficiency at full load and half load. [4]

(b) With the help of phasor diagram, derive the expression for approximate voltage regulation of a transformer at lagging power factor. Also draw the equivalent circuit of transformer. [4]

6 (a) With the help of neat diagram, explain the working principle of three phase induction motor? [4]  
 (b) With the help of neat diagram, draw and explain torque-slip characteristics three phase induction motor? Also, discuss its significance. [4]

\*\*\*\*\*END\*\*\*\*\*