

**SUPPLEMENTARY EXAMINATION** Feb-2019**CEE-201 DIGITAL CIRCUITS AND SYTEMS**

Time:3:00 Hours

Max. Marks :40

**Note:** Attempt any FIVE questions. All questions carry equal marks.  
Assume suitable missing data, if any.

1. [a] Express the following functions in a sum of minterms and a product of maxterms. 4+4

$$F(A, B, C, D) = D(\bar{A} + B) + \bar{B}D$$

- [b] Implement the following Boolean function with two and three level NOR Gates.

$$F(x, y, z) = \sum(0, 6)$$

2. [a] Design a Half adder circuit. Draw its logic diagram also. 4+4

- [b] Obtain the simplified expressions in sum of products for the following Boolean functions:

(i)  $F(A, B, C, D) = \sum(7, 13, 14, 15)$

(ii)  $F(x, y, z) = \bar{x}yz + x\bar{y}\bar{z} + xyz + xy\bar{z}$

- ~~3. [a] Implement the following functions using the don't-care conditions. Assume that both the normal and complement inputs are available. 4+4~~

$$F(A, B, C, D) = A'B'C' + AB'D + A'B'CD'$$

$$d(A, B, C, D) = ABC + AB'D'$$

With no more than two NOR gates.

- [b] Design a Half subtractor circuit. Draw its logic diagram also?

4. [a] Explain the Exclusive-OR and equivalence function for two variables using truth-table and karnaugh maps. 4+4

- [b] A combinational circuit has four inputs and one output. The output is equal to 1 when (1) all the inputs are equal to 1 or (2) none of the inputs are equal to 1 or (3) an odd number of inputs are equal to 1.

- (i) Obtain the truth table.

- (ii) Find the simplified output function in sum of products.



(iii) Find the simplified output function in product of sums.

(iv) Draw the two logic diagrams.

5. [a] A combinational circuit is defined by the following three functions:

$$F_1 = \bar{x}\bar{y} + xy\bar{z}$$

4+4

$$F_2 = \bar{x} + y$$

$$F_3 = xy + \bar{x}\bar{y}$$

Design the circuit with a decoder and external gates.

[b] Implement the Boolean function  $F(A, B, C) = \sum(1, 3, 5, 6)$  with  $4 \times 1$  multiplexer. Choose A and B as select lines.

6. Write short notes on any two of the following.

4+4

[a] Clocked RS flip flop

[b] Postulates of Ordinary algebra and Boolean algebra. Compare the Boolean algebra with arithmetic and ordinary algebra.

---[c] Combinational and Sequential Circuits

-----