

SUPPLEMENTARY EXAMINATION, FEB-2019
CEC-103 ENGINEERING ANALYSIS & DESIGN

Max. Marks: 40

Time: 3:00 Hours

Note: Attempt Any four questions! Assume suitable missing data if any.

Q.1 For the circuit shown in fig. 1, obtain an expression for the current delivered by the source as a function of time, when the switch S is closed at $t=0$. Assume the circuit to be initially unenergised. [10]

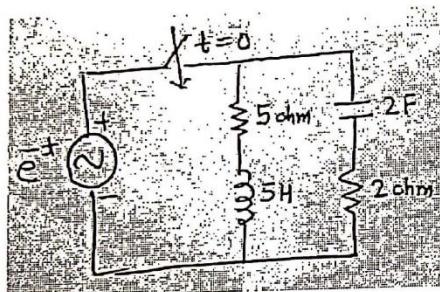


Fig. 1

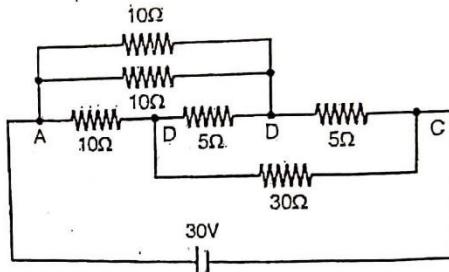


Fig. 2

Q.2 a) State and explain the superposition theorem with a suitable example. [5]
b) Find the current through the 5-ohm resistor at D-D terminal in the circuit shown in fig. 2. [5]

Q. 3 a) Obtain the impedance Z for the following circuit shown in fig. 3. [5]
b) Find the V_{th} and R_{th} at terminal A-B for the fig. 4. [5]

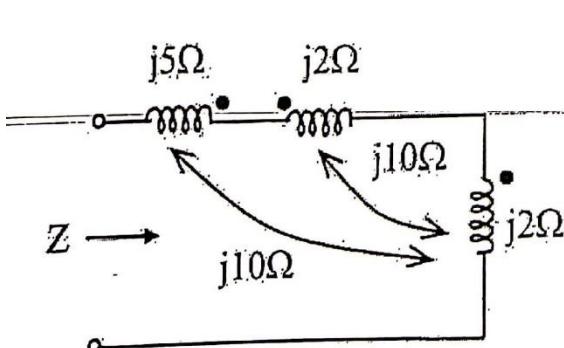


Fig. 3

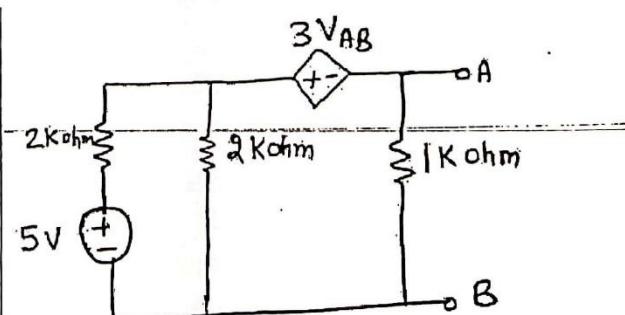


Fig. 4

- 244 -

Q.4 a) Determine $z(t) = x(t) * y(t)$, where $X(s) = \frac{1}{s+1}$ and $Y(s) = \frac{1}{s+5}$. (" * " denotes convolution operator). [5]

b) Obtain the cut-set matrix for network shown in the fig. 5 [5]

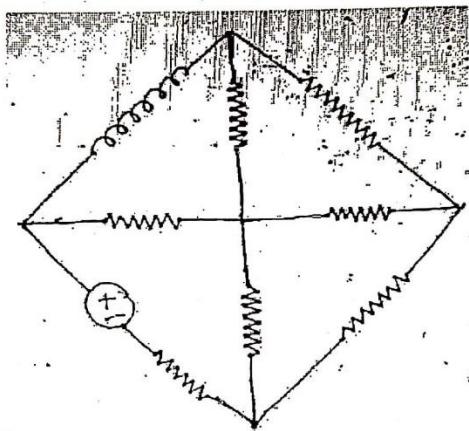


Fig. 5

Q.5 State and prove the maximum power transfer theorem with suitable example. [10]