

EC-561 DIGITAL SYSTEM DESIGN

Time: 03 Hours

Max. Marks: 100

Note: Answer all Questions, selecting at least Two from each Question. Assume suitable missing data, if any.

- 1 a) Implement 2 to 4 decoder using logic gates and write VHDL code for the same circuit using any architecture body. (10)
- b) Explain various types of delays and their modeling in VHDL with suitable examples and diagrams. (10)
- c) Explain Identifiers and Data Operators in detail with their significance. (10)
- 2 a) Implement the synchronous sequential circuit for state diagram as shown in Fig.1, using D-Flip Flop. (10)

 


Fig. 1

- b) Reduce the given state table using partitioning technique and find a minimum length that distinguishes state q₁ from state q₂. (10)

PS	NS, Z	
	X=0	X=1
q ₁	q ₂ , 1	q ₈ , 1
q ₂	q ₈ , 1	q ₄ , 1
q ₃	q ₄ , 0	q ₅ , 1
q ₄	q ₃ , 0	q ₆ , 1
q ₅	q ₄ , 1	q ₃ , 1
q ₆	q ₃ , 1	q ₇ , 1
q ₇	q ₁ , 1	q ₄ , 1
q ₈	q ₃ , 0	q ₁ , 1

- c) Explain various hazards and faults in digital circuits. Also suggest few examples with methods to make circuits hazard free. (10)

- 3 a) What are the Moore and Mealy machines? Compare them. Define: Successor, terminal state, strongly connected machine and machine equivalence. (10)
- b) What is a sequential machine? Discuss various memory elements used in sequential machines. How is the state of the memory element specified? (10)
- c) Construct the compatibility graph and obtain the minimal cover table for the sequential machine described by the state table as given below: (10)

PS	NS, Z	
	X=0	X=1
a	-	f, 0
b	b, 0	c, 0
c	e, 0	a, 0
d	b, 0	d, 0
e	f, 1	d, 0
f	a, 0	-

- 4 a) Design a synchronous sequential circuit (sequence detector) using D flip-flop, which produces an output z=1, whenever input sequence 1011 occurs. Overlapping is allowed. (10)
- b) Discuss the conversion process for Mealy to Moore machine. Convert the given Mealy state table to Moore State table: (10)

PS	NS, Z	
	X=0	X=1
A	A, 0	B, 0
B	C, 0	B, 0
C	A, 0	D, 0
D	C, 1	B, 0

- c) List various programmable logic devices. Explain full functioning of FPGA with the help of its block diagram. (10)
- 5 a) What are the elements of an ASM chart, explain each. Compare ASM Chart and Conventional flow chart in detail. (10)
- b) Draw the state diagram and ASM Chart for the sequence detector that can detect 1010 sequence. Overlapping is allowed. (10)
- c) Draw the ASM chart for the given state transitions. Start from the initial state T₁, then if xy = 00 go to T₂, if xy = 01 go to T₃, if xy = 10 go to T₁, otherwise to T₃ and design it using multiplexer control method. (10)