

EE-102 BASIC ELECTRICAL ENGINEERING

Time: 1:30 Hours

Max. Marks: 30

NOTE: Attempt ALL Questions.
Assume suitable missing data, if any.

Q.1 Answer the following :

(i) Indicate the series – parallel connections of individual elements in the circuit of Fig.1, as it is. [2]

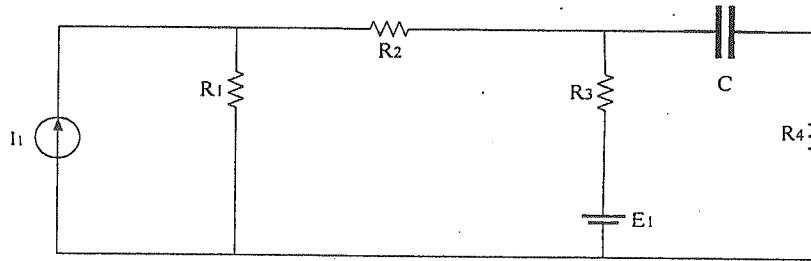


Fig. 1

(ii) Is superposition principle applicable on the following functions? Explain. [2]

a) $y = 5x^2 + 2x + 7$

b) $y = \sin x$

(iii) What are the various types of dependent sources. Draw the symbol of each. [2]

Q. 2 The voltage waveform shown in Fig. 2 is applied to a pure capacitor of 1 F. Sketch the current waveform over the specified time interval.

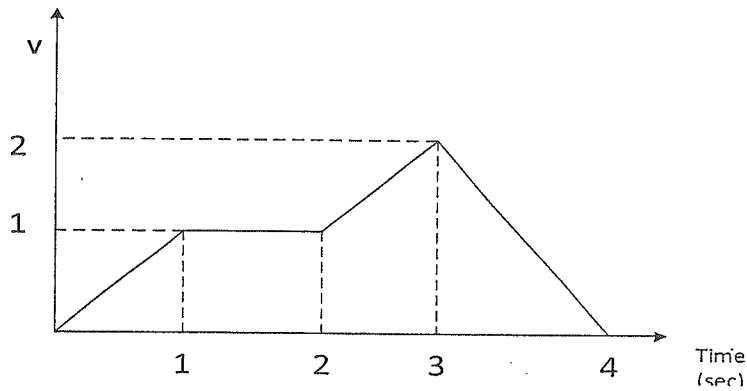


Fig. 2

[4]

Q. 3 For the network shown in Fig.3, use star – delta transformation to find voltage V that makes current $I=3A$. [4]

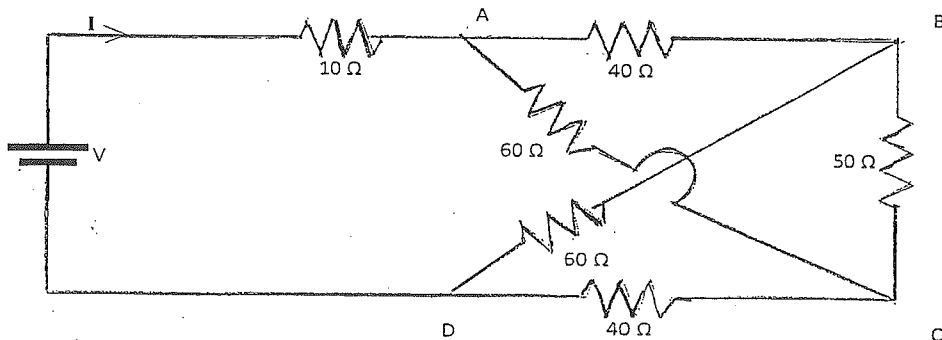


Fig. 3

Q.4 In the circuit of Fig. 4, determine the value of resistor R_L that will absorb maximum power and what is the value of this power?

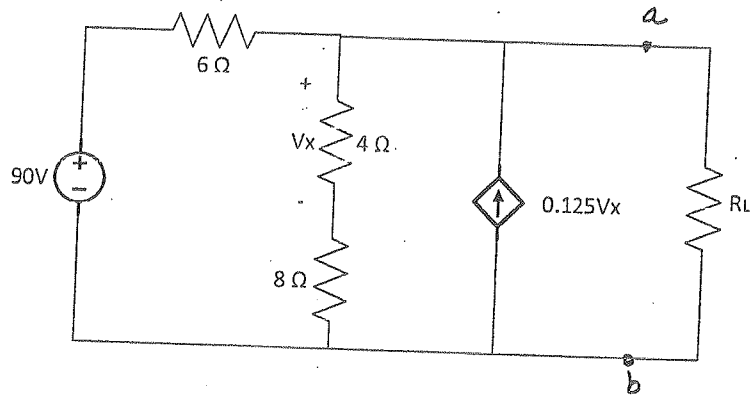


Fig. 4

Q.5 Find the average and effective values of the voltage for the waveform shown in Fig. 5.

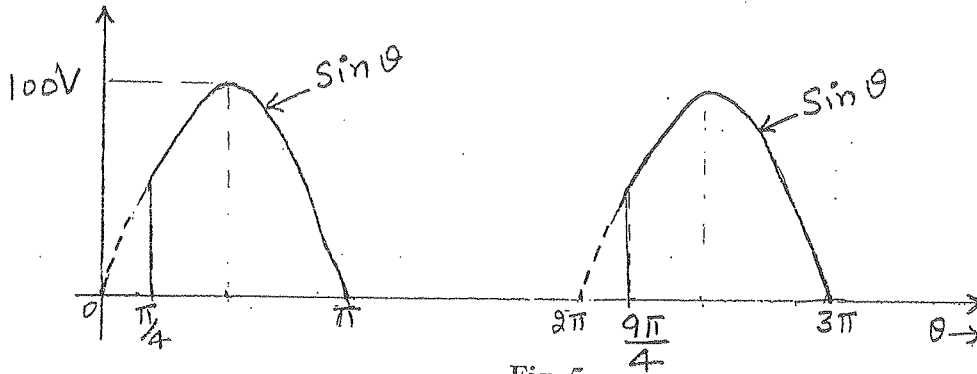


Fig. 5

Q.6 What are the characteristics of a series RLC resonance circuit. Derive the expressions of current and power at lower and upper cut-off frequencies. [4]

Q.7 The parallel circuit shown in Fig. 6 is connected across a single phase 200 V, 33.5 Hz ac supply. Calculate (i) total current (ii) power factor and (iii) draw the phasor diagram. [4]

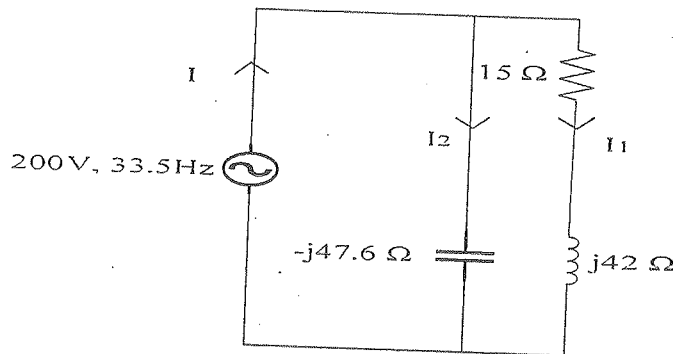


Fig. 6