

Total No. of Pages 02

- 162 -

VI SEMESTER
MID SEMESTER EXAMINATION

B.Tech. (EE/EL)
March-2019

EE-304 Power System and Analysis


Time: 1:30 Hours

Max. Marks: 20

Note : All questions are compulsory.
Assume suitable missing data, if any.


Q.1 For the transmission system in figure 2, all shunt elements are capacitors with an admittance $y_c = j0.01$ per unit, and all series elements are inductors with an impedance $z_{line} = j0.08$ per unit. Using G-S method, determine first iteration values of δ_2 , $|V_3|$, δ_3 , P_{G1} , Q_{G1} , and Q_{G2} for the system. Assume suitable acceleration factor.

6

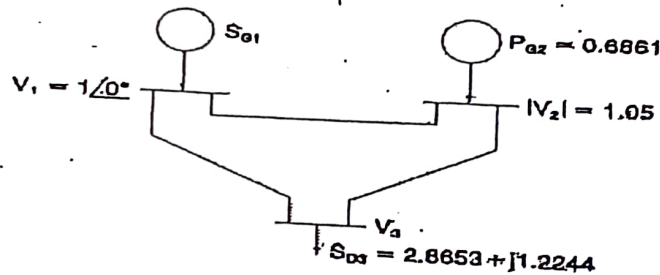


Q.2 For the following power system network, bus 1 is slack bus, bus 3 and 5 are PV buses and remaining buses are PQ buses. The first iteration of the Newton Raphson algorithm for computing power flow is given as: $[A]^1 = [B]^0 + [J]^{-1} [C]$. Fill up all the elements of the matrix J and vectors A, B and C.

4

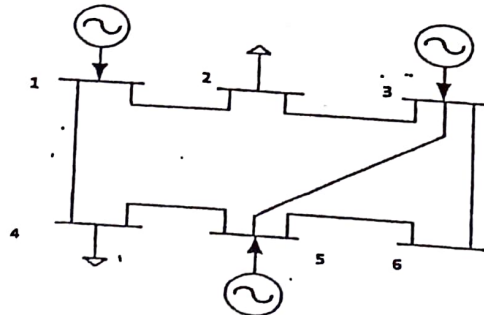

P.T.O.

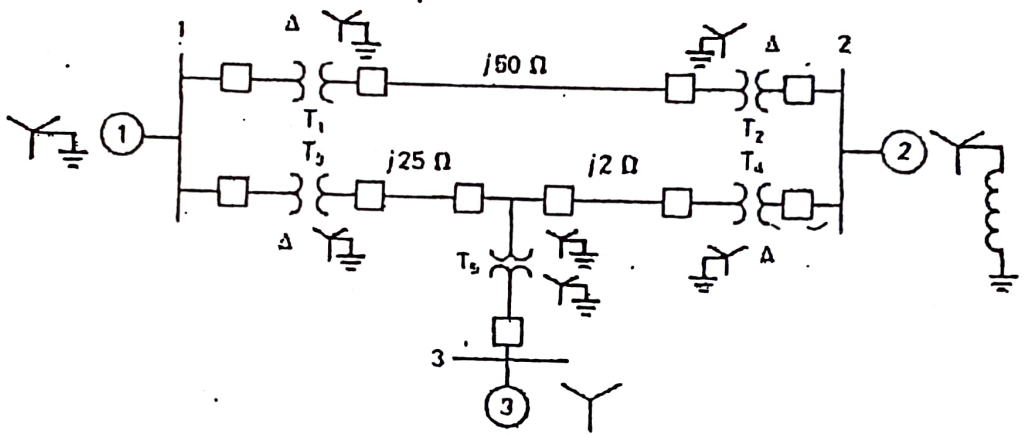Q.3. Consider the single-line diagram of the power system shown in Figure 1. Equipment ratings are:
 Generator 1: 1000 MVA, 18 kV, $X = 0.2$ per unit
 Generator 2: 1000 MVA, 18 kV, $X = 0.2$ p.u.
 Synchronous motor 3: 1500 MVA, 20 kV, $X = 0.2$ p.u.
 Three-phase Δ -Y transformers
 T1, T2, T3, T4: 1000 MVA, 500 kV Y/20 kV Δ , $X = 0.1$ p.u.
 Three-phase Y-Y transformer
 T5: 1500 MVA, 500 kV Y/20 kV Y, $X = 0.1$ p.u.
 Neglecting resistance, transformer phase shifts, and magnetizing reactance, draw the equivalent reactance diagram. Use a base of 100 MVA and 500 kV for the 50-ohm line. Determine the per-unit reactances. 5



Q.4 Form Y_{Bus} matrix for the 6 bus system as per the data given below. 5

From Bus	To Bus	R pu	X pu	$Y_{ch} / 2$ pu
1	2	0.10	0.20	$j 0.02$
1	4	0.05	0.20	$j 0.02$
1	5	0.08	0.30	$j 0.03$
2	3	0.05	0.25	$j 0.03$
2	4	0.05	0.10	$j 0.01$
2	5	0.10	0.30	$j 0.02$
2	6	0.07	0.20	$j 0.025$
3	5	0.12	0.26	$j 0.025$
3	6	0.02	0.10	$j 0.01$
4	5	0.20	0.40	$j 0.04$
5	6	0.10	0.30	$j 0.03$