

No. of Pages 03

Semester VI

End Semester Examination

Time: 1:30 Hours

Roll No.....

B. Tech (EL/EE/EC/EP)

March-2019

Maximum Marks: 20


EE-322 ADVANCED ANALOG CIRCUIT DESIGN

Note: Answer any SEVEN questions.


All questions carry equal marks.

Assume suitable value for missing data (if any).

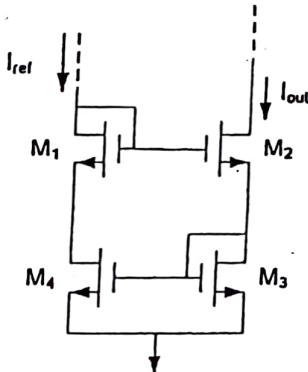- 1 Determine the output resistance of the modified Wilson current mirror circuit given below. 03



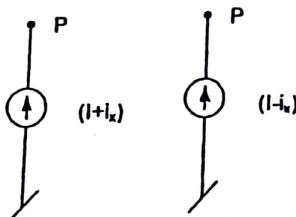- 2 With the help of current mirrors realize the following types of current sources where the point P can be at arbitrary potential. 02




- 3 Draw the complete circuit of the output stage of the op-amp IC741 (without the short-circuit protection transistors and resistors). Using appropriate analysis determine the bias current (collector) for all the transistors used in the output stage. Take $I_{Ref} = 720 \mu A$, $\beta_{PNP} = 50$ and $\beta_{NPN} = 200$, $I_{s14} = I_{s20} = 3 \times 10^{-16} A$. 2.5

4 Draw the intermediate stage of the op-amp IC741 and carryout a small signal analysis to determine the (i) transconductance of this stage and (ii) input impedance of this stage. Clearly mention any simplifying assumptions made in the analysis.

2.5 X 2


5 Explain the translinear circuit principle as applicable for circuits consisting of BJTs. Using this principle determine the value of $\frac{I_{O2}-I_{O1}}{I_{IZ}-I_{T1}}$, for the circuit shown below.

03

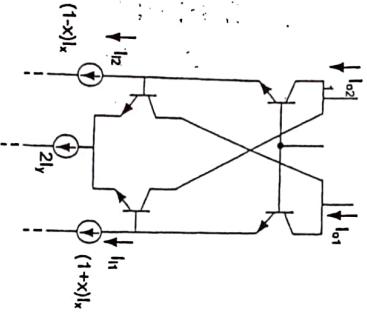

- 165 -

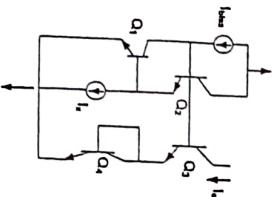6 Determine the output current I_{O1} for the circuit shown below: 02



Write short notes on any TWO of the following:

- (a) Supply current sensing method
- (b) Slew rate phenomenon in Operational amplifiers
- (c) Cascode current mirror
- (d) Instrumentation amplifier design using the supply current sensing method